

### Chapter 3

#### Node Analysis

无 Voltage source (n nodes)

S1. select a node as the reference node

S2. Assign node voltages  $v_1, \dots, v_{n-1}$  to the remaining nodes (nonreference)

S3. Apply KCL to each of the nonreference nodes

有 Voltage source 且只有 independent current source (n+1 nodes)

"Node Analysis by Inspection"

对 n 个 nonreference nodes: 列 node-voltage matrix equations

$$\begin{bmatrix} G_{11} & G_{12} & \dots & G_{1n} \\ G_{21} & G_{22} & \dots & G_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ G_{n1} & G_{n2} & \dots & G_{nn} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_n \end{bmatrix} = \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_n \end{bmatrix}$$

$G_{kk}$ : Sum of the conductances connected to node k

$G_{kj} = G_{jk}$ : Negative of the sum of the conductances directly connecting nodes k & j

$i_k$ : Sum of all independent current sources directly connected to node k, 流入的记为正

$$Gv = i$$

conductance matrix      output vector      input vector

有 Voltage source (both dependent & independent)

Case 1: Voltage source 与 reference node 相连 -- 已知非reference node 的电压

Case 2: Voltage source 连在两个 nonreference nodes 间

S2 把这个 voltage source, 两个 nodes 和与之直接并到的元件组成一个 supernode, 对这个 supernode 列 KCL

S1 列:  $v_k - v_j = \text{Voltage source}$

Linear: Output linearly related to input: homogeneity & additivity

nonlinear element example: diode (二极管)

$$i_D = I_S (e^{qV_D/RT} - 1) \quad I_S, q, k, T \text{ 为 value \& means}$$


解 nonlinear 超方法: 正常微分方程按线性化 (See cot slide 9)

Superposition principle: When a linear system is driven by more than one independent source, the total output = the sum of individual outputs

Application:

Remove Independent sources, Leave dependent sources intact! All but one "0" at a time.

#### Source Transformation

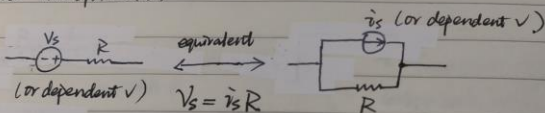

#### Thevenin's Theorem

A linear two-terminal circuit  $\leftrightarrow$   $V_{Th}$  in series with  $R_{Th}$

where  $V_{Th}$ : 开路时  $V_{ab}$

$R_{Th} = R_{eq}$  (with all independent sources off) 横向

无 dependent source: turn off sources, 求  $R_{eq}$   
有 dependent source: turn off independent sources

例如电压源  $V_0$ , 得电流  $i_0$

$$R_{Th} = R_{eq} = \frac{V_0}{i_0}$$

$R_{Th}$  can be negative -- implies that the circuit is supplying power

#### Mesh Analysis

适用于 planar circuit

无 Current Sources

S1. Assign mesh currents  $i_1, \dots, i_n$  to the n meshes (按取顺时针)

S2. Apply KVL to each of the n meshes

(公共部分电流 --  $i_k - i_j$ )

有 Current Sources 且只有 independent voltage sources

"Mesh Analysis by Inspection"

列 mesh-current equations

$$\begin{bmatrix} R_{11} & R_{12} & \dots & R_{1n} \\ R_{21} & R_{22} & \dots & R_{2n} \\ \vdots & \vdots & \ddots & \vdots \\ R_{n1} & R_{n2} & \dots & R_{nn} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_n \end{bmatrix} = \begin{bmatrix} v_1 \\ v_2 \\ \vdots \\ v_n \end{bmatrix}$$

$R_{kk}$ : Sum of the resistances in mesh k

$R_{kj} = R_{jk}$ : Negative of the sum of the resistances in common with meshes k & j

$v_k$ : Sum taken clockwise of all independent voltage sources in mesh k, with voltage rise taken as positive 与 KVL 相反

有 Current Sources (both dependent & independent)

Case 1: A current source exists only in one mesh -- 已知该 mesh current  $i_k$

Case 2: A current source exists between two meshes

S1: 这两个 mesh 电流满足:  $i_k - i_j = \text{current source}$

S2: 把这两个 mesh 去掉公共部分后所得的视为一个 supermesh 对这个 supermesh 列 KVL

#### Power transfer

two objectives

power utility systems: Large quantities  
communication sys: Small amount

major concern: Efficiency  
Power transfer

$$P = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L \xrightarrow{\text{max}} \frac{V_{Th}^2}{4R_{Th}}$$

"I" for load      Thevenin's Theorem


#### Source Modeling

Practical voltage source



$R_s$  越小越 ideal

Practical current source

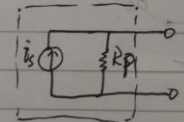

$R_p$  越大越 ideal

unloaded source voltage/current  
loading effect